

Report must of Computer Science Design Logic

Experiment 2: Simulation

$$(A'B + C') (AB'C' + B) (AB' + C')$$

Truth table.

A	B	C	A'B	A'B + C'	AB'	AB' + C'	AB'C' + B	Y
0	0	0	0	1	0	1	1	0
0	0	1	0	1	0	1	1	0
0	1	0	1	1	0	0	0	0
0	1	1	1	1	0	0	0	0
1	0	0	0	0	1	1	1	0
1	0	1	0	0	1	1	1	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0

Department of Computer Science Design Logic

Component 2: Simulation

$$(A'B + C') (AB'C' + B)' (AB' + C')$$

Truth table.

A	B	C	A'B	A'B + C'	AB'	AB' + C'	AB'C' + B'	Y
0	0	0	0	1	0	1	1	1
0	0	1	0	1	0	0	1	0
0	1	0	1	1	0	1	0	0
0	1	1	1	0	0	0	0	0
1	0	0	0	0	1	1	1	0
1	0	1	0	1	1	1	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	1	0	0	0	0

Component 3:

1) (a) Converting to Binary

$$M_{16} \times F_{16}$$

$$M_{16} \rightarrow 0100\ 1100$$

$$M_{16} \rightarrow 01001100_2$$

$$F \rightarrow 1111$$

Binary multiplication of $4C_{16} \times F_{16}$

$$\begin{array}{r}
 0100 \times 0100 \ 1100 \times 1111 \\
 \hline
 0100 \ 1100 \\
 010001 \ 100 \times \\
 010001100 \times \times \\
 010001100 \times \times \times \\
 \hline
 10001110100
 \end{array}$$

$$\therefore (10001110100)_2$$

(u) BCD arithmetic operation

$$\begin{array}{r}
 287 - 331 \text{ [Using 10's complement]} \\
 A \quad \quad B
 \end{array}$$

10's complement of a number is 1 added to its 9's complement number

$$\begin{array}{r}
 9's \text{ comp of } 331 \rightarrow \begin{array}{r} 999 \\ - 331 \\ \hline 668 \end{array}
 \end{array}$$

$$\text{adding : } 668 + 1 = 669.$$

① Adding 10's complement to 287

$$\begin{array}{r} 287 \\ + 669 \\ \hline 956 \end{array}$$

as there is no carry answer is (-287)

$$\begin{array}{r} 999 \\ - 956 \\ \hline 43 \end{array}$$

$$\text{adding } 1 = 43 + 1 = 44$$

$$\therefore 287 - 331 = -44 \quad \text{using 10's complement Method.}$$



2) De Morgan's theorem

$$(AB)' = A' + B'$$

Complement of product of two variables is equal to sum of variables is equal to sum of complements of individual variables

Circuit diagram

$$(AB)' = A' + B'$$

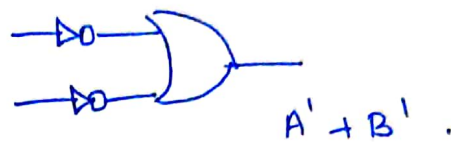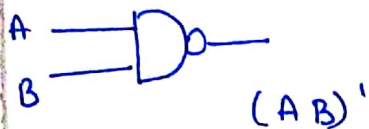

Truth table.

A	B	AB	$(AB)'$	A'	B'	$A' + B'$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

(1)

(2)

Hence proved,



$$(AB)' = A' + B'$$

$$(A+B)' = A' \cdot B'$$

Complement of sum of two variables is equal to the product of complement of individual variables.

Circuit diagram:

$$(A+B)' = A' \cdot B'$$

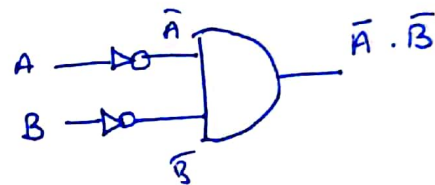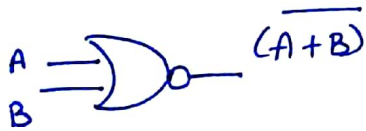

Truth table.

A	B	A+B	$(A+B)'$	A'	B'	$A' \cdot B'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

(1)

(2)

Hence proved LHS = RHS

$$(A+B)' = A' \cdot B'$$

4

4) $F(A, B, C, D) = \pi(0, 1, 2, 4, 5, 7, 11, 15)$

CD	00	01	11	10
AB				
00	0 0	0 1	1 3	0 2
01	0 4	0 5	0 7	1 6
11	1 12	1 13	0 15	1 14
10	1 8	1 9	0 11	1 10

$$(0, 1, 2, 4, 5) \rightarrow \bar{A} \cdot \bar{C}$$

$$(0, 2) \rightarrow \bar{A} \bar{B} \bar{D}$$

$$(5, 7) \rightarrow \bar{A} B D$$

$$(11, 15) \rightarrow A \cdot C D$$

$$\bar{Y} = \bar{A} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot \bar{D} + \bar{A} \cdot B D + A \cdot C D$$

$$\bar{Y} = \bar{A} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot \bar{D} + \bar{A} \cdot B D + A \cdot C D$$

$$Y = (A + C)(A + B + D) \cdot (A + B' + D')$$

$$(A' + C' + D')$$

5) Full Adder using Half adder.

Block diagram, ckt, Expression, IT

Block diagram:




Truth table:

A	B	Cin	Sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}
 \text{Sum} &= A'B'C + A'BC + AB'C' + ABC \\
 &= C(A'B' + AB) + C'(A'B + AB') \\
 &= C \text{ XOR } (A \text{ XOR } B)
 \end{aligned}$$
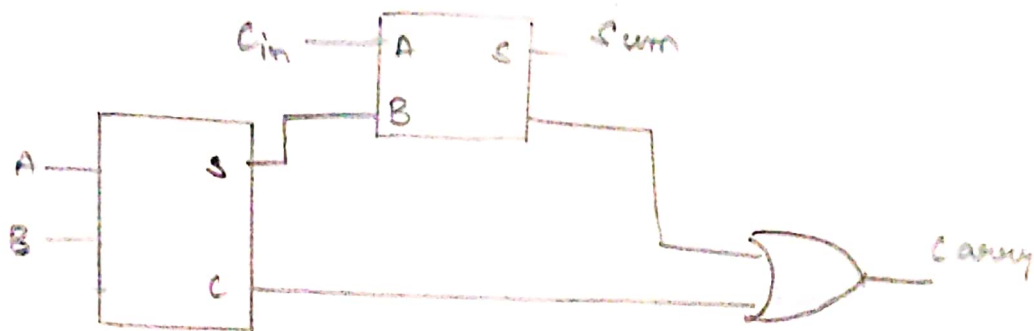
$$\begin{aligned} \text{Carry} &= A'BC + AB'C + ABC + ABC \\ &= AB + BC + AC. \end{aligned}$$



Using NAND only

